

# Digital Logic Theoretical Assignment 3 Solution

1.

State Equation:

$$A(t+1) = J_A A' + K'_A A = (Bx + B'y')A' + (B'xy')'A$$

$$B(t+1) = J_B B' + K'_B B = (A'x)B' + (A + xy')'B$$

Output Equation:

$$z = Ax'y' + Bx'y'$$

State and Output Table

Present State		Input		Next State		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>y</i>	<i>A</i>	<i>B</i>	<i>z</i>
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

Also, you can use FF's inputs to derive state table, instead of using state equations


$$A(t+1) = J_A A' + K'_A A$$

$$B(t+1) = J_B B' + K'_B B$$

$$z = Ax'y' + Bx'y'$$

Current State		Input		Flip-Flop Inputs				Next State		Output
A(t)	B(t)	x	y	$J_A$	$K_A$	$J_B$	$K_B$	A(t+1)	B(t+1)	z
0	0	0	0	1	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	1	1	1	1	0
0	0	1	1	0	0	1	0	0	1	0
0	1	0	0	0	0	0	0	0	1	1
0	1	0	1	0	0	0	0	0	1	0
0	1	1	0	1	0	1	1	1	0	0
0	1	1	1	1	0	1	0	1	1	0
1	0	0	0	1	0	0	1	1	0	1
1	0	0	1	0	0	0	1	1	0	0
1	0	1	0	1	1	0	1	0	0	0
1	0	1	1	0	0	0	1	1	0	0
1	1	0	0	0	0	0	1	1	0	1
1	1	0	1	0	0	0	1	1	0	0
1	1	1	0	1	0	0	1	1	0	0
1	1	1	1	1	0	0	1	1	0	0

**State Diagram:**

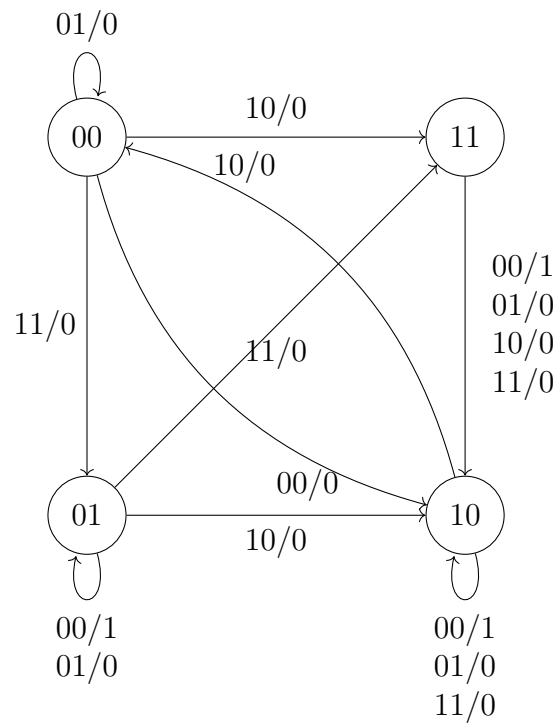

**2.**

**Input Equation:**

$$T_A = A + B$$

$$T_B = A' + B$$

**State Equation:**


$$A(t+1) = A \oplus T_A = A \oplus (A + B)$$

$$B(t+1) = B \oplus T_B = B \oplus (A' + B)$$

**State Table:**

Present State		Next State	
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>
0	0	0	1
0	1	1	0
1	0	0	0
1	1	0	0

**State Diagram:**

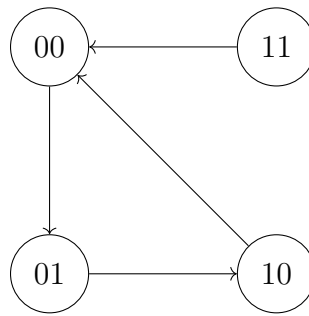

**3.**

a)

**Input Equation:**

$$J_1 = X$$

$$J_2 = X$$

$$K_1 = (XQ_2)'$$

$$K_2 = (XQ_1)'$$

**State Equation:**

$$Q_1(t+1) = J_1Q_1' + K_1'Q_1 = XQ_1' + XQ_1Q_2'$$

$$Q_2(t+1) = J_2Q_2' + K_2'Q_2 = XQ_2' + XQ_1Q_2$$

**Output Equation:**

$$F = X \oplus Q_2'$$

**State Table:**

Present State		Input	Next State		Output
$Q_1$	$Q_2$	$X$	$Q_1$	$Q_2$	$F$
0	0	0	0	0	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Also, you can use FF's inputs to derive state table, instead of using state equations


$$Q_1(t+1) = J_1 Q_1' + K_1' Q_1$$

$$Q_2(t+1) = J_2 Q_2' + K_2' Q_2$$

$$F = X \oplus Q_2'$$

Current State		Input	Flip-Flop Inputs				Next State		Output
$Q_1(t)$	$Q_2(t)$	X	$J_1$	$K_1$	$J_2$	$K_2$	$Q_1(t+1)$	$Q_2(t+1)$	F
0	0	0	0	1	0	1	0	0	1
0	0	1	1	0	1	1	1	1	0
0	1	0	0	1	0	1	0	0	0
0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	0	0	1
1	0	1	1	0	1	0	1	1	0
1	1	0	0	1	0	1	0	0	0
1	1	1	1	1	1	0	0	1	1


### State Diagram:

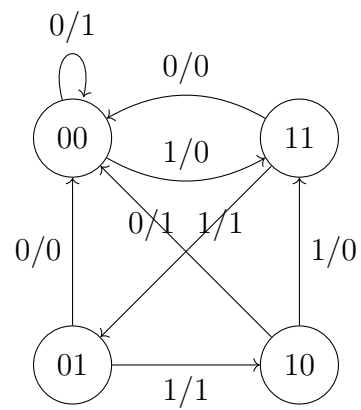

b)

This is a Mealy machine, because the output is determined by the input and the present state. For example, when the present state is 00, the output is different when the input is 0 or 1.

c)

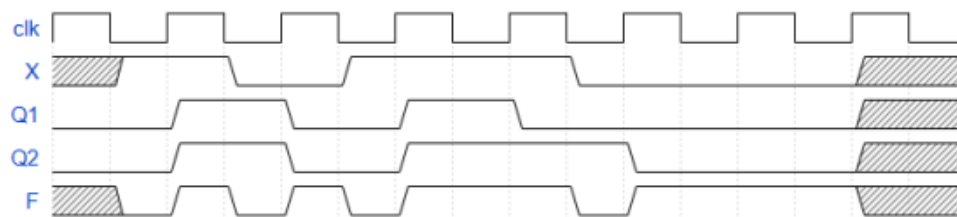

## 4. Simplified Version

State Table:

Present State	Input	Next State
$Q$	$X$	$Q$
$a$	0	$b$
$a$	1	$a$
$b$	0	$d$
$b$	1	$c$
$c$	0	$d$
$c$	1	$c$
$d$	0	$a$
$d$	1	$d$

Reduced State Table:

Present State	Input	Next State
$Q$	$X$	$Q$
$a$	0	$b$
$a$	1	$a$
$b$	0	$d$
$b$	1	$b$
$d$	0	$a$
$d$	1	$d$

Let  $a = 00$ ,  $b = 01$ ,  $d = 10$ , then the reduced state table is: **State Table with TFF**  
**Input:**

Present State		Input	Next State		TFF Input	
$Q_1$	$Q_2$	$X$	$Q_1$	$Q_2$	$T_1$	$T_2$
0	0	0	0	1	0	1
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	0	1	1	0	0	0
1	1	0	X	X	X	X
1	1	1	X	X	X	X

Derive Input Equation:

		$Q_2 \backslash Q_1$			
		00	01	11	10
$Q_1$	0	0	0	0	1
	1	1	0	X	X

$T_1$

		$Q_2 \backslash Q_1$			
		00	01	11	10
$Q_1$	0	1	0	0	1
	1	0	0	X	X

$T_2$

$$T_1 = Q_1 X' + Q_2 X'$$

$$T_2 = Q_1' X'$$



## 4. Non-Simplified Version

State Table:

Present State	Input	Next State
$Q$	$X$	$Q(t+1)$
$a$	0	$b$
$a$	1	$a$
$b$	0	$d$
$b$	1	$c$
$c$	0	$d$
$c$	1	$c$
$d$	0	$a$
$d$	1	$d$

Let  $a = 00$ ,  $b = 01$ ,  $c = 10$ ,  $d = 11$  then the reduced state table is: **State Table with TFF Input:**

Present State		Input	Next State		TFF Input	
$Q_1$	$Q_2$	$X$	$Q_1$	$Q_2$	$T_1$	$T_2$
0	0	0	0	1	0	1
0	0	1	0	0	0	0
0	1	0	1	1	1	0
0	1	1	1	0	1	1
1	0	0	1	1	0	1
1	0	1	1	0	0	0
1	1	0	0	0	1	1
1	1	1	1	1	0	0

Derive Input Equation:

$Q_1 \backslash Q_2$	00	01	11	10
0	0	0	1	1
1	0	0	0	1

$T_1$

$Q_1 \backslash Q_2$	00	01	11	10
0	1	0	1	0
1	1	0	0	1

$T_2$

$$T_1 = Q_1'Q_2 + Q_2X'$$

$$T_2 = Q_2'X' + Q_1'Q_2X + Q_1X'$$

5.

State Table:


Present State		Input		Next State
$Q$		$En$	$D$	$Q$
0	0	0	0	0
0	0	0	1	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

Derive Input Equation:

$Q$	$EnD$			
	00	01	11	10
0	0	0	1	0
1	1	1	1	0

$$Q(t+1) = EnD + QEn'$$

Block Diagram:

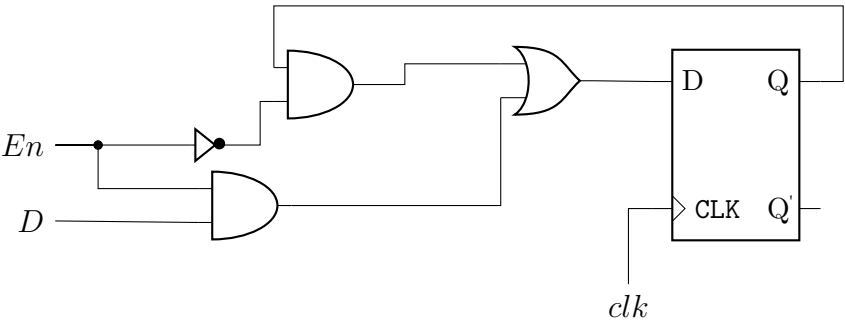

6.

a)

Characteristic Table:

$A$	$B$	$Q(t + 1)$	Operation
0	0	0	Reset
0	1	$Q(t)$	No Change
1	0	$Q(t)'$	Complement
1	1	1	Set

b)

State Table:

Current State	Input		Next State
$Q$	$A$	$B$	$Q$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

**Simplify Characteristic Equation:**

$Q \backslash AB$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Q(t+1) = Q'A + QB$$

c)

**Excitation Table:**

$Q(t)$	$Q(t+1)$	$A$	$B$	Operation
0	0	0	X	No Change
0	1	1	X	Set
1	0	X	0	Reset
1	1	X	1	No Change

d)

**State Table with JKFF Input:**

Current State		JKFF Input		Next State	New FF Input	
$Q$		$J$	$K$	$Q$	$A$	$B$
0	0	0	0	0	0	X
0	0	0	1	0	0	X
0	1	0	0	1	1	X
0	1	1	1	1	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	0	1	X	1
1	1	1	1	0	X	0

**Simplify New FF Input:**

$Q \backslash JK$	00	01	11	10
0	0	0	1	1
1	X	X	X	X

$A$

$Q \backslash JK$	00	01	11	10
0	X	X	X	X
1	1	0	0	1


$B$

The simplified JKFF input is:

$$A = J$$

$$B = K'$$

**Block Diagram:**

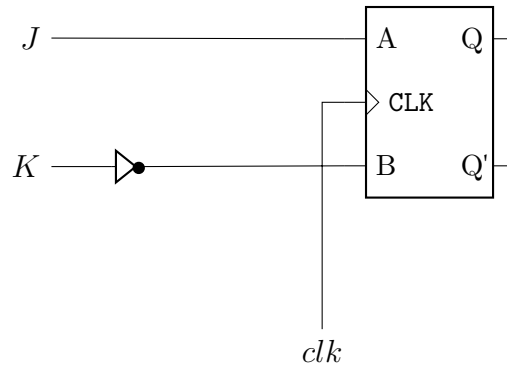


**7.**

**Reduced State Table:**

Present State	Next State		Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$a$	$f$	$b$	0	0
$b$	$d$	$a$	0	0
$d$	$g$	$a$	1	0
$f$	$f$	$b$	1	1
$g$	$g$	$d$	0	1

**State Diagram:**

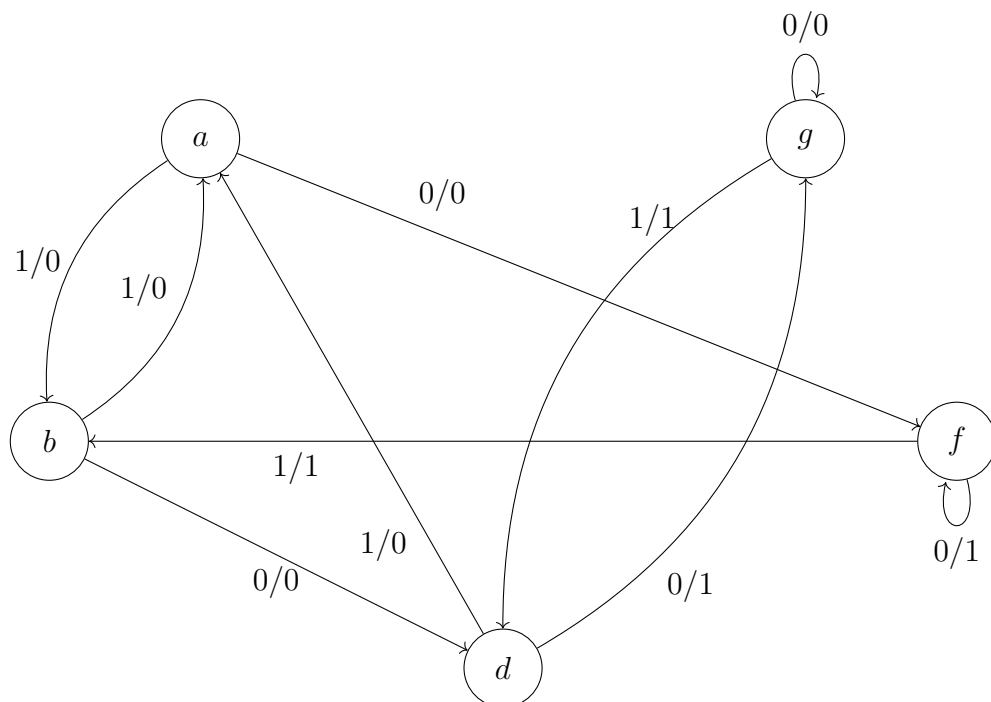

Let  $a = 000$ ,  $b = 001$ ,  $d = 010$ ,  $f = 011$ ,  $g = 100$ .

**State Table with JKFF Input:**

Present State			Input	Next State			JKFF Input						Output
$Q_1$	$Q_2$	$Q_3$	$X$	$Q_1$	$Q_2$	$Q_3$	$J_1$	$K_1$	$J_2$	$K_2$	$J_3$	$K_3$	$F$
0	0	0	0	0	1	1	0	X	1	X	1	X	0
0	0	0	1	0	0	1	0	X	0	X	1	X	0
0	0	1	0	0	1	0	0	X	1	X	X	1	0
0	0	1	1	0	0	0	0	X	0	X	X	1	0
0	1	0	0	1	0	0	1	X	X	1	0	X	1
0	1	0	1	0	0	0	0	X	X	1	0	X	0
0	1	1	0	0	1	1	0	X	X	0	X	0	1
0	1	1	1	0	0	1	0	X	X	1	X	0	1
1	0	0	0	1	0	0	X	0	0	X	0	X	0
1	0	0	1	0	1	0	X	1	1	X	0	X	1
1	0	1	0	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

**Simplify JKFF Input:**

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	X	X	X	X
10	X	X	X	X

$J_1$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

$K_1$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	1	0	0	1
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

$J_2$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	X	X
01	1	1	1	0
11	X	X	X	X
10	X	X	X	X

$K_2$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	1	1	X	X
01	0	0	X	X
11	X	X	X	X
10	0	0	X	X

$J_3$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	1	1
01	X	X	0	0
11	X	X	X	X
10	X	X	X	X

$K_3$


The simplified JKFF input is:

$$\begin{aligned}
 J_1 &= Q_2 Q'_3 X' \\
 J_2 &= Q'_1 X' + Q_1 X \\
 J_3 &= Q'_1 Q'_2
 \end{aligned}$$

$$\begin{aligned}
 K_1 &= X \\
 K_2 &= Q'_3 + X \\
 K_3 &= Q'_2
 \end{aligned}$$

8.

State Diagram:

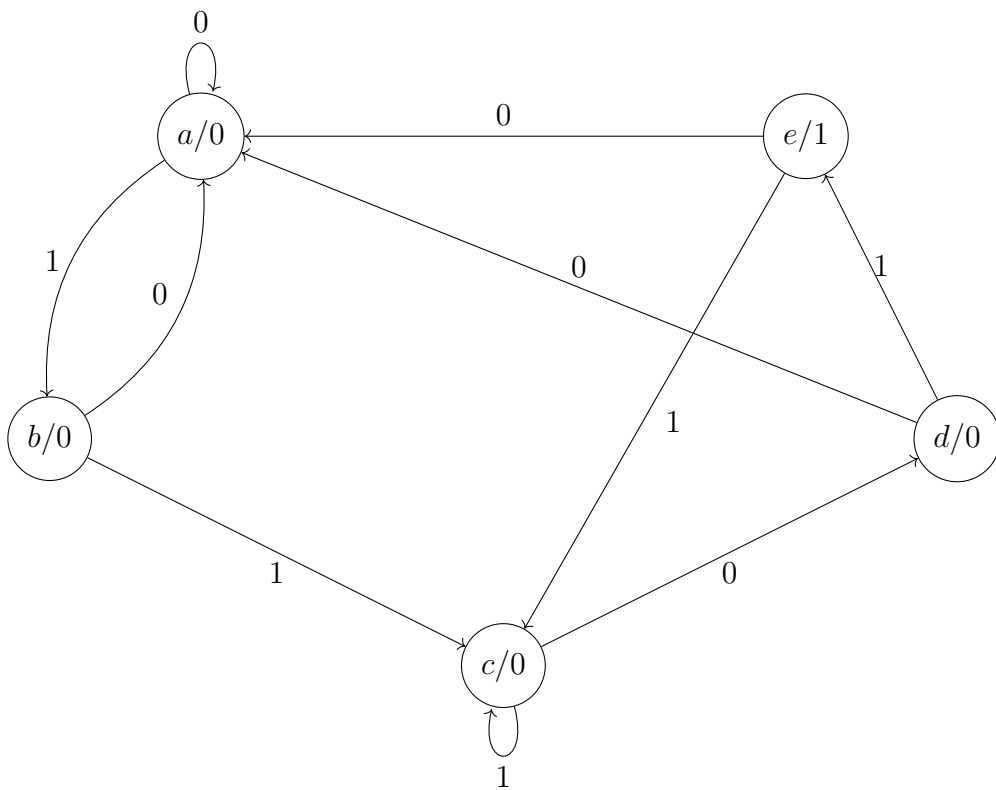

Let  $a = 000$ ,  $b = 001$ ,  $c = 010$ ,  $d = 011$ ,  $e = 100$ .

State Table with DFF Input:

Present State			Input $X$	Next State			DFF Input		
$Q_1$	$Q_2$	$Q_3$		$Q_1$	$Q_2$	$Q_3$	$D_1$	$D_2$	$D_3$
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0	1	0
0	1	0	0	0	1	1	0	1	1
0	1	0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	1	0
1	0	1	0	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X



### Simplify DFF Input:

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$D_1$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	1	0
01	1	1	0	0
11	X	X	X	X
10	0	1	X	X

$D_2$

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	X	X	X	X
10	0	0	X	X

$D_3$

The simplified DFF input is:

$$D_1 = Q_2 Q_3 X$$

$$D_2 = Q_2 Q_3' + Q_1 X + Q_2' Q_3 X$$

$$D_3 = Q_2 Q_3' X' + Q_1' Q_2' Q_3' X$$

