

# DIGITAL LOGIC

## Chapter 4 part3: Arithmetic Circuit


2023 Fall



# Today's Agenda

- Recap
- Context
  - Binary Adder-Subtractor
  - Decimal Adder
  - Binary Multiplier
- Reading: Textbook, Chapter 4.5-4.7

# Recap

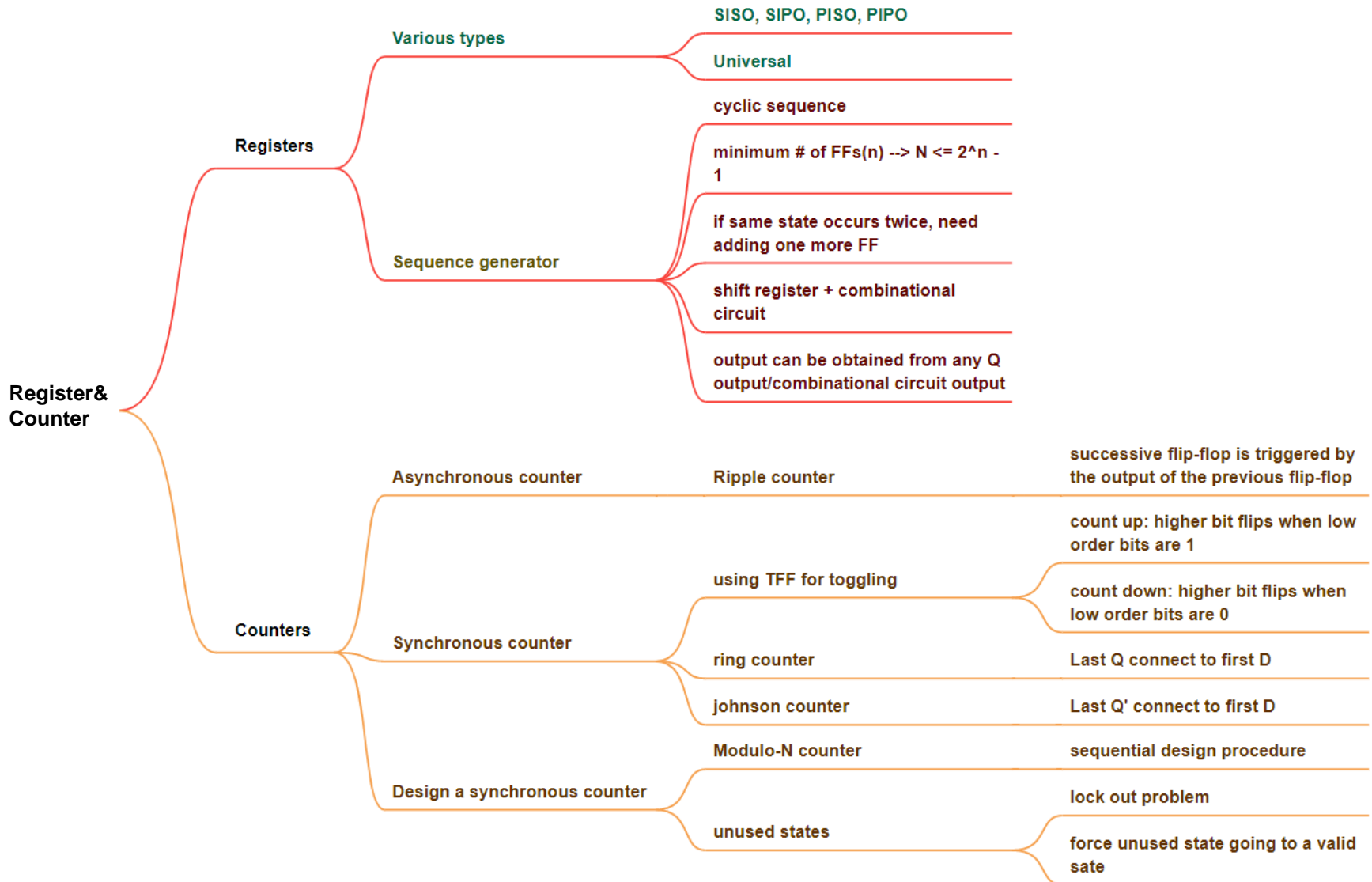



# Outline

- **Binary Adder**
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions

# Binary Add

- Similar to the addition operation of decimal numbers.
- $0+0 = 0$ ,  $0+1 = 1$ ,  $1+0 = 1$ ,  $1+1 = 10$  ← The higher significant bit is called a **carry** (进位).
- A combinational circuit that performs the addition of two bits as described above is called a **half-adder**.
- The addition operation involves three bits — the **augend bit**, **addend bit**, and the **carry bit** and produces a sum result as well as carry.
- The combinational circuit performing this type of addition operation is called a **full-adder**.

11	carry(进位)
1011	augend(被加数)
0001	addend(加数)
<hr/>	
1100	sum

# Recall: Design Procedure

1. Specification: From the specifications, determine the inputs, outputs, and their symbols.
2. Formulation: Derive the truth table (functions) from the relationship between the inputs and outputs
3. Optimization: Derive the simplified Boolean functions for each output function. Draw a logic diagram for the resulting circuits using AND, OR, and inverters.
4. Technology Mapping: Transform the logic diagram to a new diagram using the available implementation technology.
  - Verification: Verify the design.

# Half-adder

- 1. Spec

- Inputs:  $x, y$
- Outputs:  $C$ (carry),  $S$ (sum)

- 2. Truth table



		$2^1$	$2^0$
$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- 3. Boolean function


$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

- 4. Block diagram

  

# Full-adder

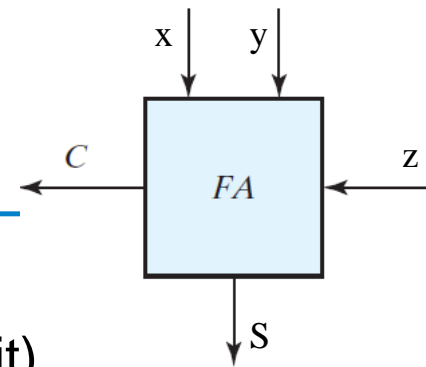

- 1. Spec
  - Inputs:  $x$ ,  $y$ ,  $z$  (carry from previous lower significant bit)
  - Outputs:  $C$  (carry),  $S$  (sum)


## 2. Truth table

## 3. Boolean function


$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

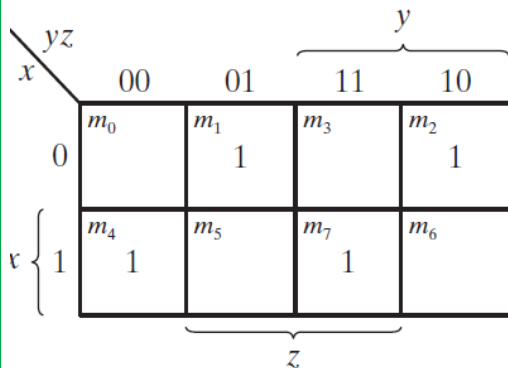

(a)  $S = x'y'z + x'yz' + xy'z' + xyz$

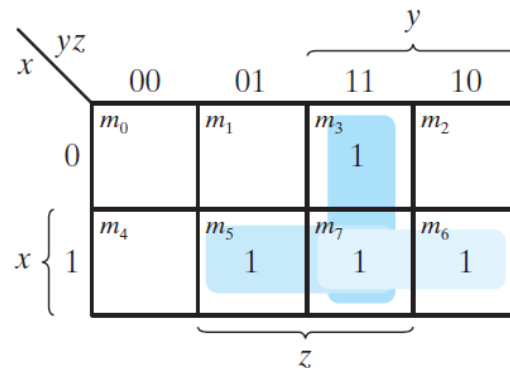

(b)  $C = xy + xz + yz$

xor gate, odd number  
of 1  $\rightarrow$  sum = 1

if  $\geq$  two inputs are 1  
 $\rightarrow$  carry = 1





# Full-adder

- 3. Boolean function

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

- 4. Block diagram

 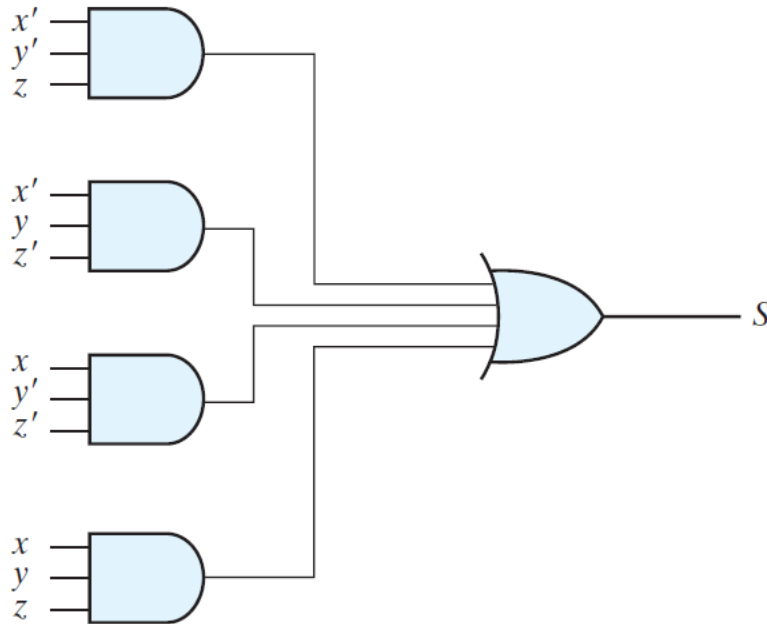





# Full Adder Implemented with Half Adders

- Full adder implemented with: Two half adders and one OR gate

$$\begin{aligned} S &= xy'z' + x'yz' + xyz + x'y'z \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z \oplus (x \oplus y) \end{aligned}$$

$$C = z(xy' + x'y) + xy = z(x \oplus y) + xy$$
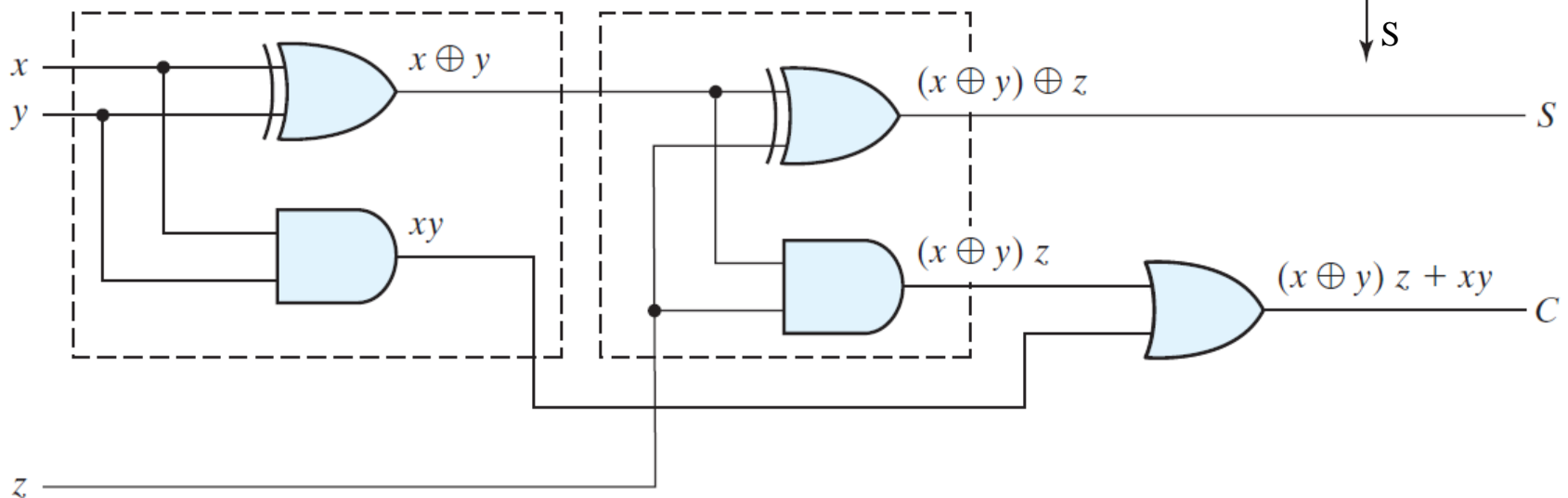 
$$\begin{aligned} S &= x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z \\ C &= xy + xz + yz \end{aligned}$$




# Ripple-Carry Adder



- unsigned addition
- $(C_n S_{n-1} S_{n-2} \dots S_0) = (A_{n-1} A_{n-2} \dots A_0) + (B_{n-1} B_{n-2} \dots B_0)$
- eg.  $S = A + B$ ,  $A = A_3 A_2 A_1 A_0$ ,  $B = B_3 B_2 B_1 B_0$ ,  $S = S_3 S_2 S_1 S_0$

The computation time of a ripple-carry adder grows linearly with word length  $n$

$T = O(n)$  due to **carry chain**

 

# Ripple-Carry Adder


Ai \ BiCi	00	01	11	10
	$m_0$	$m_1$	$m_3$	$m_2$
0		1		1
1	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$

$$S_i = A_i \oplus B_i \oplus C_i$$

Ai \ BiCi	00	01	11	10
	$m_0$	$m_1$	$m_3$	$m_2$
0			1	
1		1	1	1

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Ai	Bi	Ci	Ci+1	Si
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

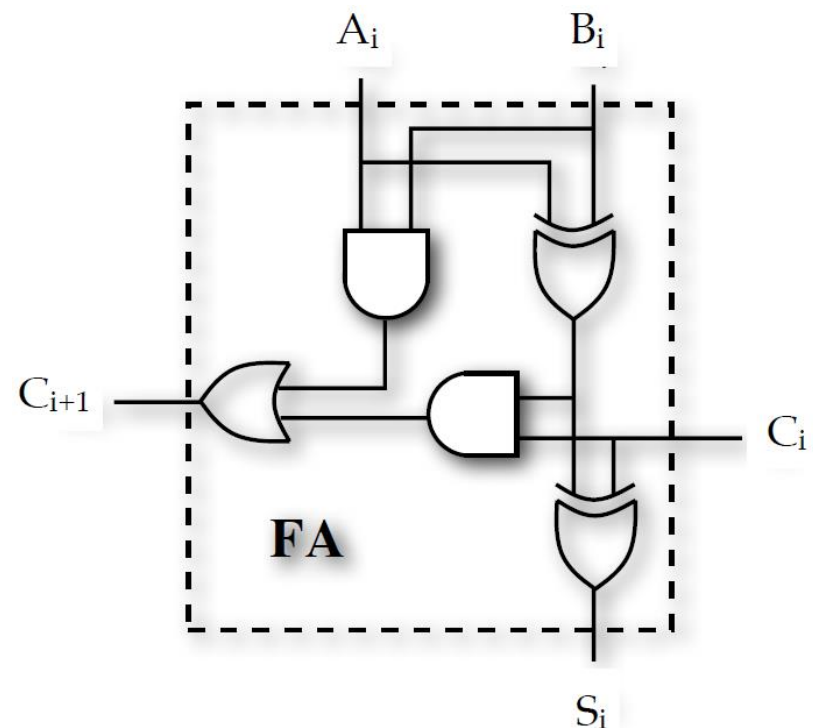

# Carry Lookahead Adder

- For a full adder, define what happens to carry

- Carry-generate:  $C_{out}=1$  independent of  $C_{in}$

- $G_i = A_i \cdot B_i$

- Carry-propagate:  $C_{out}=C_{in}$


- $P_i = A_i \oplus B_i$  or  $P_i = A_i + B_i$

$A_i$	$B_i$	$G_i$	$P_i$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	x

- Use the above  $G_i$  and  $P_i$

- $C_{i+1} = A_i B_i + B_i C_i + A_i C_i = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$

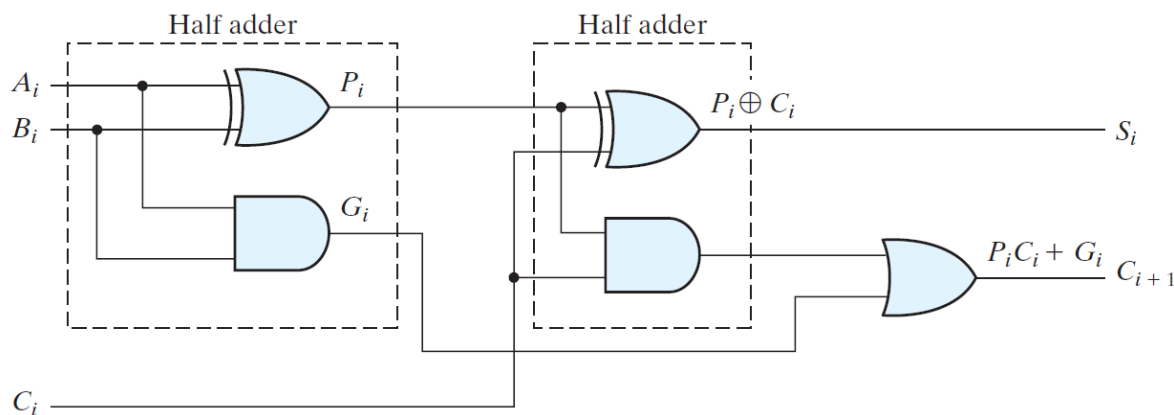- $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$



# Carry Lookahead Adder

- Do not have to wait for  $C_i$  to compute  $C_{i+1}$ 
  - $C_{i+1} = G_i + P_i C_i$
  - $C_{i+2} = G_{i+1} + P_{i+1} C_{i+1} = G_{i+1} + P_{i+1} G_i + P_{i+1} P_i C_i$
  - $C_{i+3} = G_{i+2} + P_{i+2} C_{i+2} = G_{i+2} + P_{i+2} G_{i+1} + P_{i+2} P_{i+1} G_i + P_{i+2} P_{i+1} P_i C_i$
  - $C_{i+4} = G_{i+3} + P_{i+3} C_{i+3} = G_{i+3} + P_{i+3} G_{i+2} + P_{i+3} P_{i+2} G_{i+1} + P_{i+3} P_{i+2} P_{i+1} G_i + P_{i+3} P_{i+2} P_{i+1} P_i C_i$
- Fixed delay time for each carry (but not the same for every gate!)
- Fanout of  $G_i$  &  $P_i$  also affect the overall delay → usually be limited to 4 bits

$C_0$  = input carry,

$C_1 = G_0 + P_0 C_0$ ,

$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$ ,

$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

# Carry Lookahead Adder

$C_0$  = input carry,



$C_1 = G_0 + P_0 C_0$ ,

$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$ ,

$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

$$G_i = A_i \cdot B_i$$
 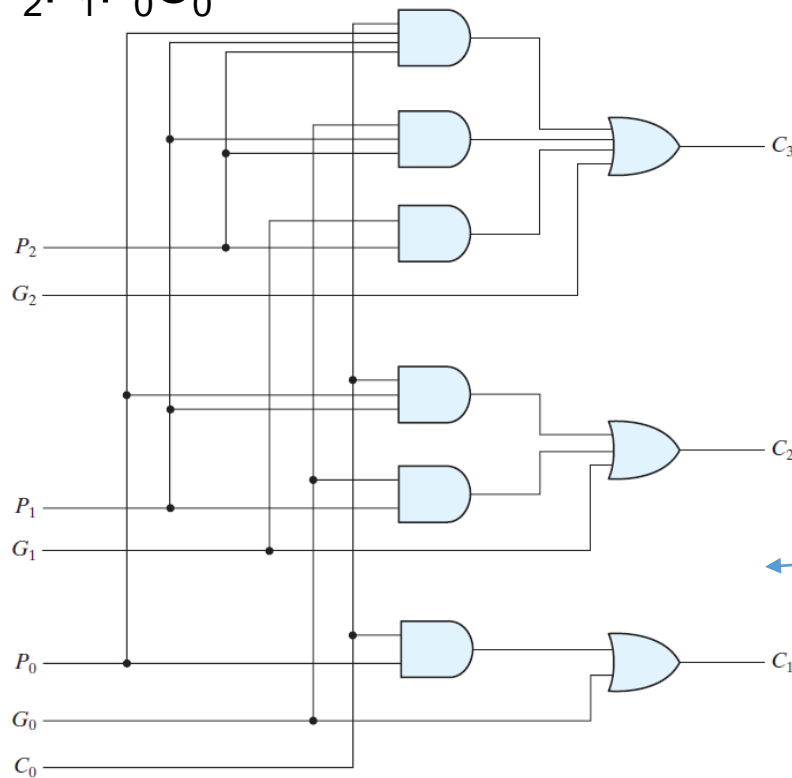
$$P_i = A_i \oplus B_i \text{ or } P_i = A_i + B_i$$





# Outline


- Binary Adder
- **Binary Subtractor**
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions



# Binary Adders/Subtractors

- Binary subtraction normally is performed by adding the minuend to the 2's complement of the subtrahend.

M	Function	Comments
0	$S=A+B$	addition
1	$S=A+B'+1$	subtraction

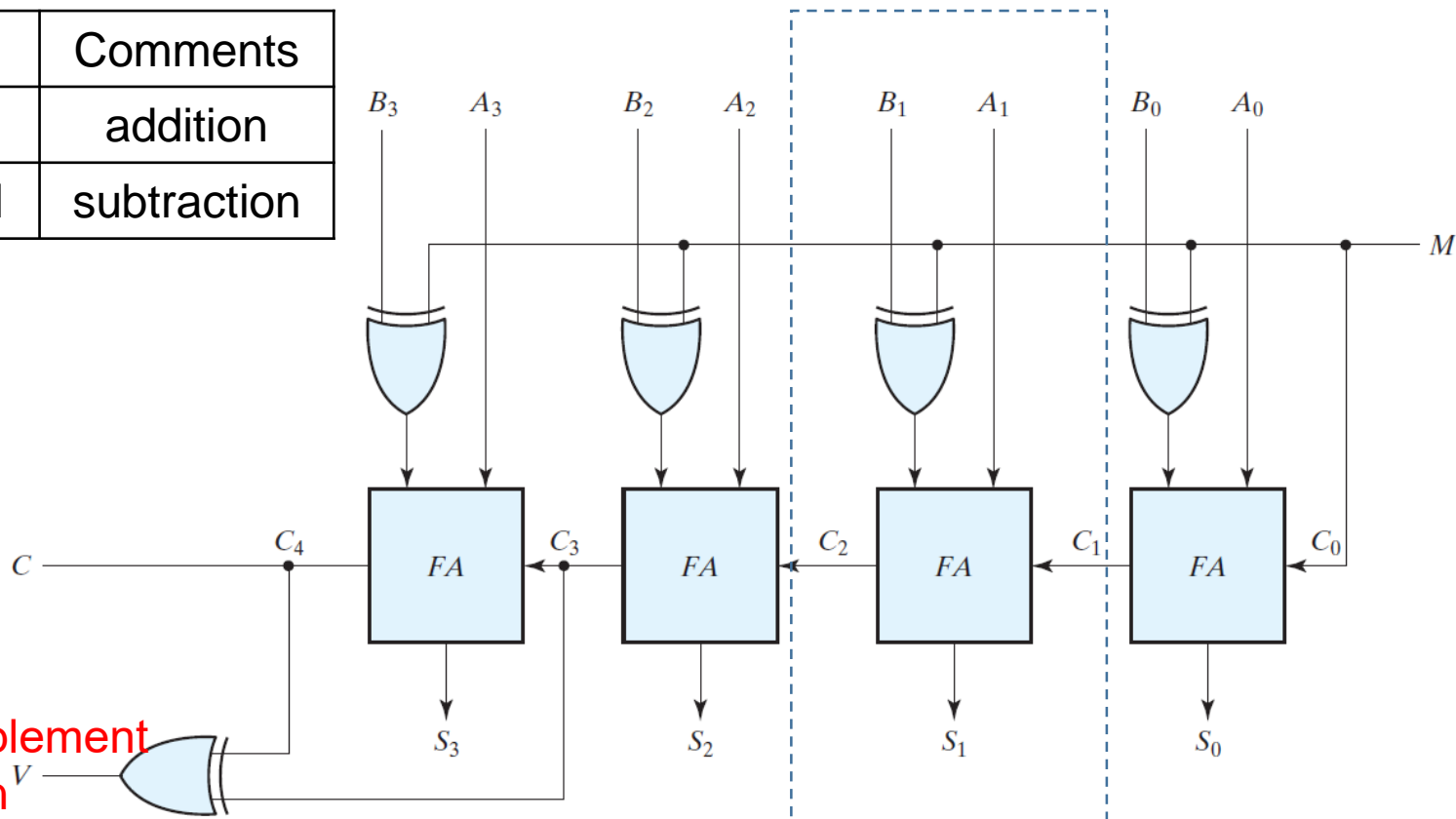

# Overflow

- When n-digits addition with sum occupying n+1 digits, we say that an overflow (溢出) occurred.

- Carry** for unsigned numbers:

- Carry indicates unsigned number overflow

$$\begin{array}{r}
 \text{1 1 1} \\
 1\ 0\ 1\ 1\ \dots\ 11 \\
 +\ 0\ 1\ 1\ 1\ \dots\ 7 \\
 \hline
 1\ 0\ 0\ 1\ 0\ \dots\ 18\ \text{(needs 5bits)}
 \end{array}$$

- Overflow** for Signed numbers: (2's Complement)

- two -ve numbers are added and the obtained result is +ve
- two +ve numbers are added and the obtained result is -ve

$$\begin{array}{r}
 \text{1 0 0 1} \\
 1\ 0\ 0\ 1\ \dots\ -7 \\
 +\ 1\ 1\ 0\ 1\ \dots\ -3 \\
 \hline
 1\ 0\ 1\ 1\ 0\ \dots\ -10 \\
 \underbrace{\hspace{1.5cm}}_6
 \end{array}$$


4 bits can not correctly represent -10

$$\begin{array}{r}
 \text{0 1 1 1} \\
 0\ 1\ 1\ 1\ \dots\ 7 \\
 +\ 0\ 0\ 0\ 1\ \dots\ 1 \\
 \hline
 1\ 0\ 0\ 0\ \dots\ 8 \\
 \underbrace{\hspace{1.5cm}}_{-8}
 \end{array}$$

4 bits can not correctly represent +8
 
# Binary Adders/Subtractors


- Overflow happens when A and B are 2's complement signed value
- Example: In each case, determine the values of the four SUM outputs, the carry C, and overflow V



M	A	B	SUM	C	V
0	0111	0110	1101	0	1
1	1100	1000	0100	1	1
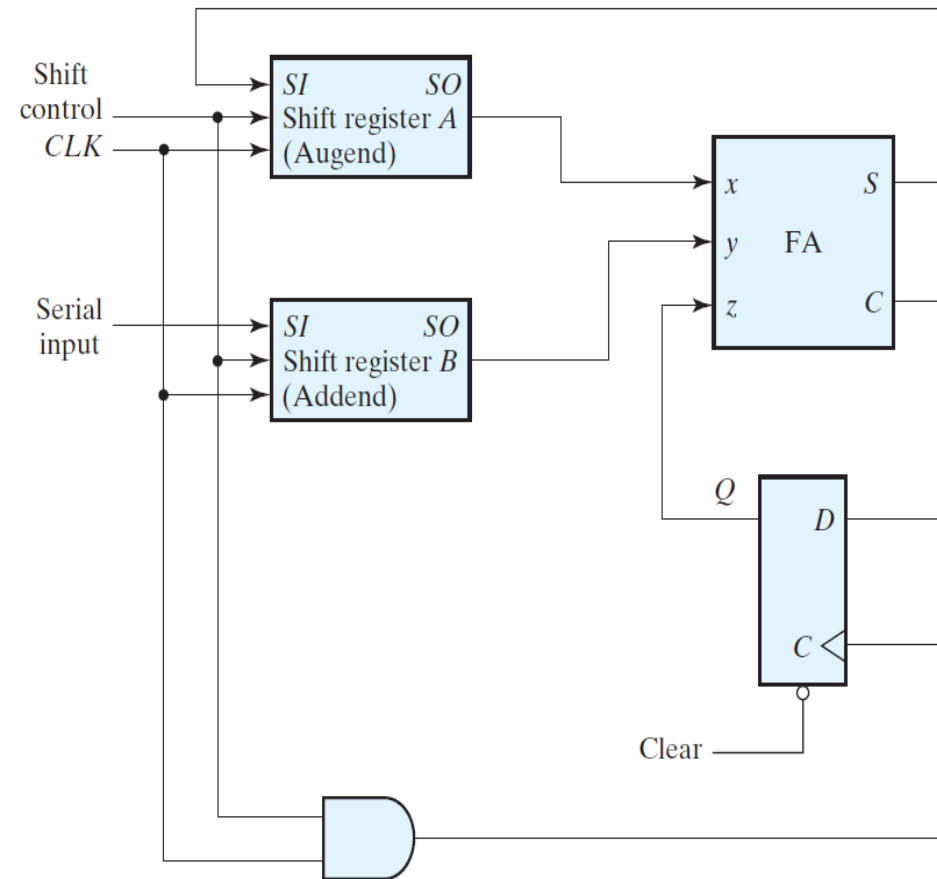
# Serial Adder

- Initially, augend is in register A and addend is in register B
- Shift control enables/disables the clock for FF
- addition of two operands from LSB to MSB
- A new sum (S) bit is transferred to shift register A
- A carry-out (C) of the FA is transferred to Q as the z input of the next addition
- Finally, when the shift control is disabled, summation result is stored in shift register A




# Timing Sequence of Serial Adder

- Serial addition of 0101 + 0111

- Register A (Store Augend and Sum): 0101
- Register B (Store Addend): 0111
- More cycles required to initialize Register A and B
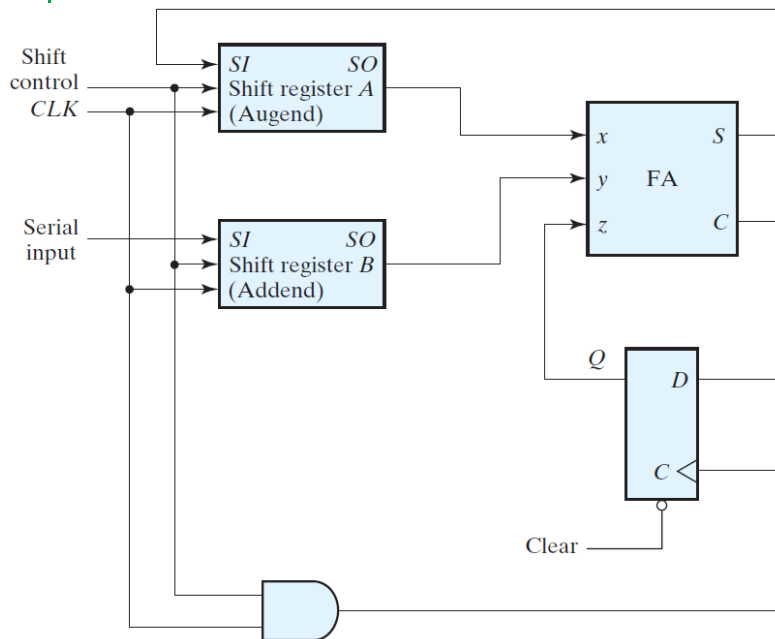
$$\begin{array}{r}
 1110 \\
 0101 \\
 + 0111 \\
 \hline
 1100
 \end{array}$$



T	Register A	Register B	C	S
0	0101	0111	0	0
1	0010	0011	1	0
2	0001	0001	1	1
3	1000	0000	1	1
4	1100	0000	0	0

sum



# Outline

- Binary Adder
- Binary Subtractor
- **Decimal Adder (BCD)**
- Binary Multiplier
- Other Arithmetic Functions

# Decimal Adders

- Addition of 2 decimal digits in BCD
- $\{C_{out}, S\} = A + B + C_{in}$
- $S = S_8 S_4 S_2 S_1$ ,  $A = A_8 A_4 A_2 A_1$ ,  $B = B_8 B_4 B_2 B_1$
- A digit in BCD cannot exceed 9, add 6 (0110) for final correction.

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

10		1 0 0 0 0	
$8_{10}$	A	1 0 0 0 <sub>2</sub>	
$9_{10}$	B	1 0 0 1 <sub>2</sub>	
<hr/>			
	KZ	1 0 0 0 1 <sub>2</sub>	binary coded results
		0 1 1 0 <sub>2</sub>	if > 9, add 6
17 <sub>10</sub>	CS	0 0 0 1 0 1 1 1 <sub>2</sub>	BCD coded result

K: binary carry, Z: binary sum, C: BCD carry, S: BCD sum

# Decimal Adders

K	Binary Sum				C	BCD Sum				Decimal
	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>		S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

$Z_8 Z_4 + Z_8 Z_2$

K


- C = 1 when
  1. K=1
  2. or K = 0, but  $A+B > 9$ , which is  $Z_8 Z_4 + Z_8 Z_2$
- C = 1 means need to add 0110

Z <sub>2</sub> Z <sub>1</sub> / Z <sub>8</sub> Z <sub>4</sub>	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1


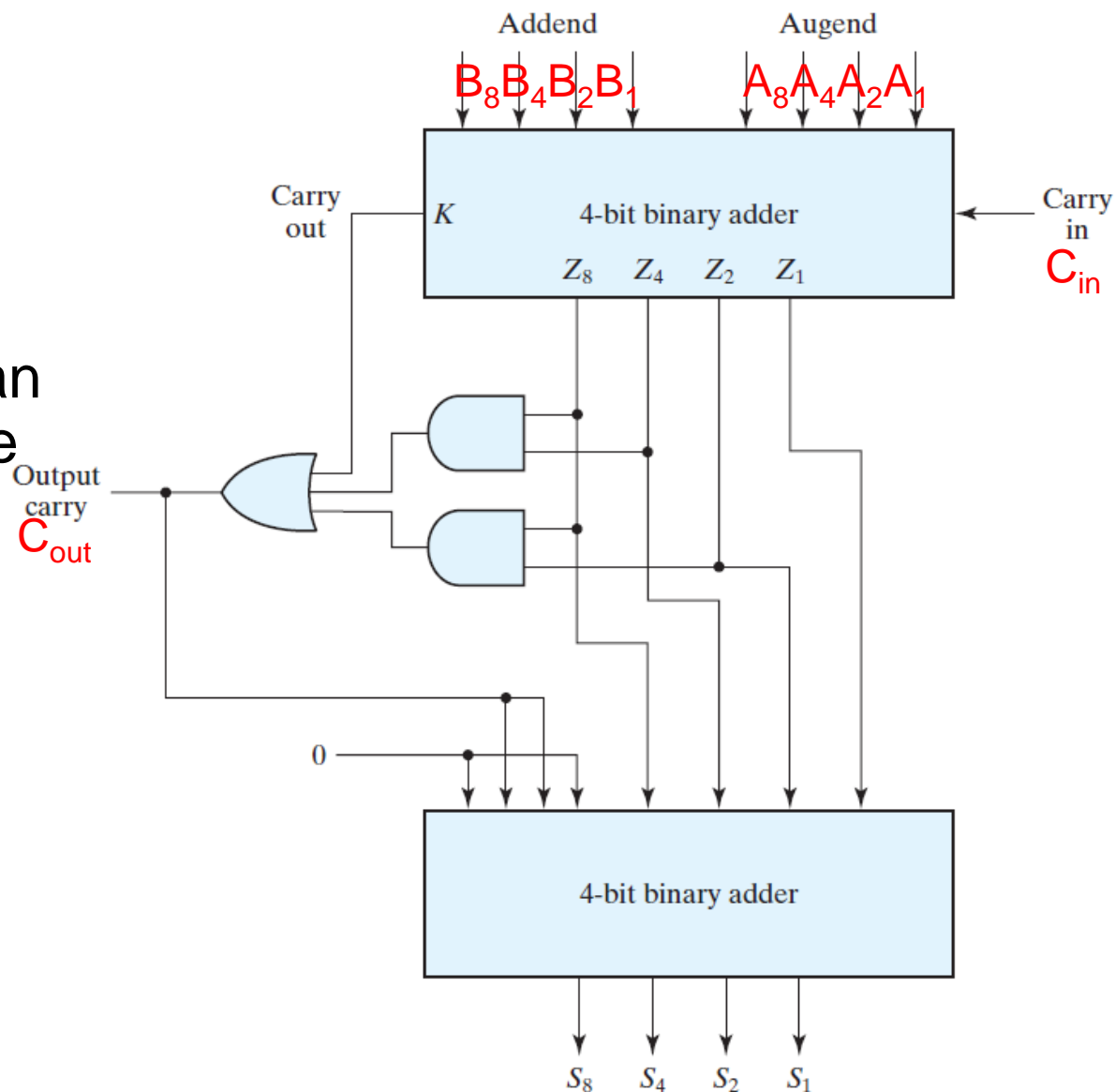
# Decimal Adders

- $C_{out} = K + Z_8 Z_4 + Z_8 Z_2$
- When  $C = 1$ , it is necessary to add 0110 to the binary sum and provide an output carry for the next stage.






# Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- **Binary Multiplier**
- Other Arithmetic Functions



## 2-bit x 2-bit Binary Multiplier

# 4-bit x 3-bit Binary Multiplier

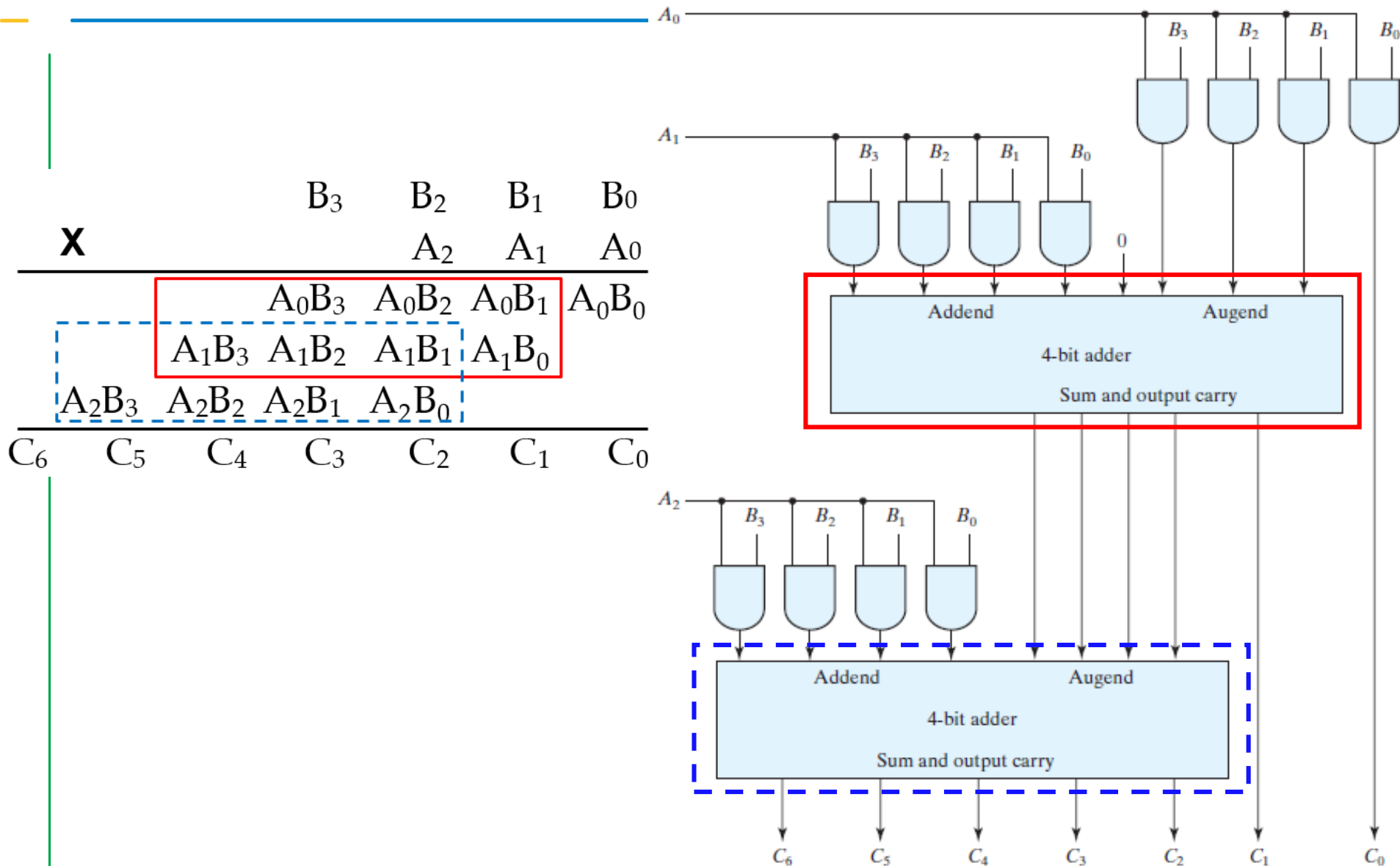



# Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- **Other Arithmetic Functions (optional)**

# Other Arithmetic Functions

- It is convenient to design the functional blocks by **contraction**
  - Removal of redundancy from circuit to which input fixing has been applied
- Functions
  - Increment
  - Decrement
  - Multiplication by constant
  - Division by constant
  - Zero fill and extension


# Design by Contraction

- Simplify the logic in a functional block to implement a different function
  - The new function must be realizable from the original function by applying basic functions to its inputs
  - Contraction is treated here only for application of 0s and 1s (not for  $X$  and  $X'$ )
  - After application of 0s and 1s, equations or the logic diagram are simplified



 
# Design by Contraction Example

- Contraction of a ripple carry adder to incrementer for  $n=1$  ( $A_2A_1A_0+001$ )



(a)

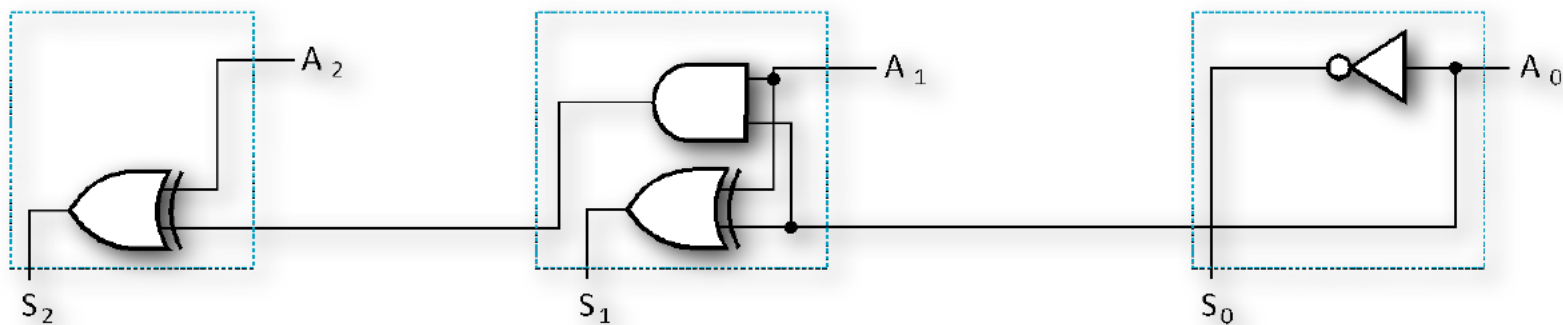




# Incrementing and Decrementing


- Incrementing
  - Add a fixed value to an arithmetic variable
  - Fixed value is often 1, called counting up
    - $A+1$ ,  $B+4$
  - Functional block is called incrementer
- Decrementing
  - Subtracting a fixed value from an arithmetic variable
  - Fixed value is often 1, called counting down
    - $A-1$ ,  $B-4$
  - Functional block is called decrementer
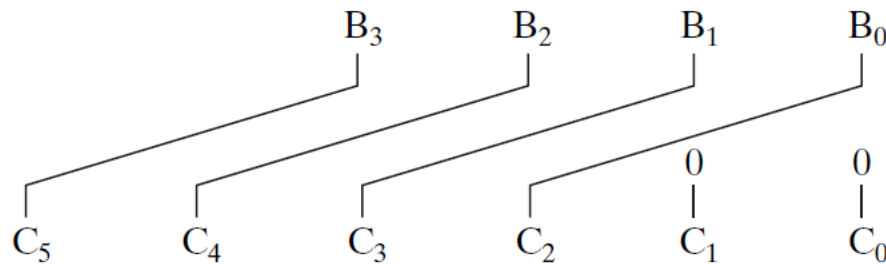
# Multiplication/Division by $2^n$

- Shift left (multiplication) or right (division)




shift left by 2

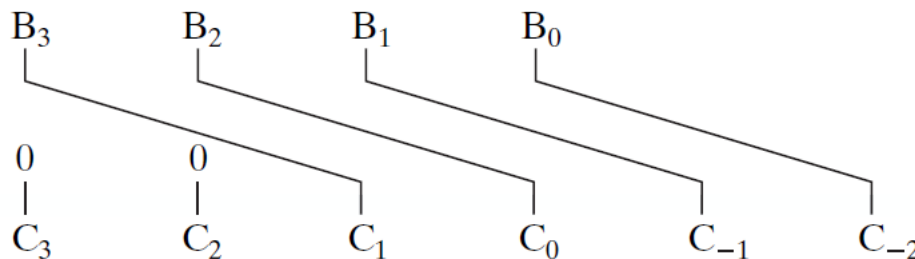

shift right by 2
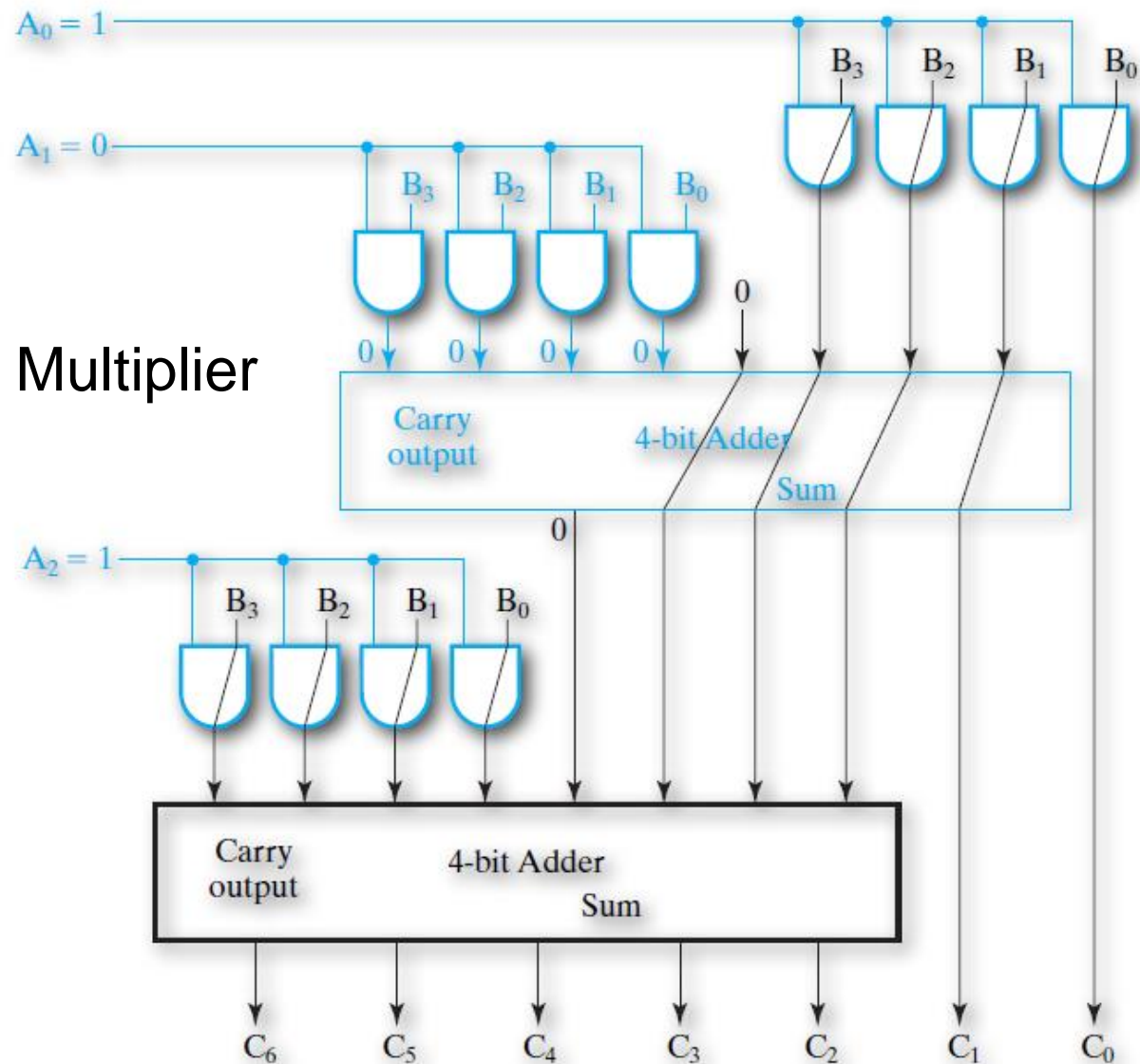
# Multiplication by a Constant

- 4-bit x 3-bit Binary Multiplier
- $B_3B_2B_1B_0 \times 101$



# Zero/Sign Extension

- Fill an m-bit operand with 0s to become an n-bit operand with  $n > m$ 
  - Filling usually is applied to the MSB end of the operand
- Zero Extension
  - 01110101 filled to 16 bits
    - 0000000001110101  $\{\{8\{0\}\}01110101\}$
  - 11110101 filled to 16 bits
    - 0000000011110101  $\{\{8\{0\}\}11110101\}$
- Sign Extension
  - Copies the MSB of the operand into the new positions
  - 01110101 extended to 16 bits
    - 0000000001110101  $\{\{8\{a7\}\}a71110101\}$
  - 11110101 extended to 16 bits
    - 1111111111110101  $\{\{8\{a7\}\}a71110101\}$